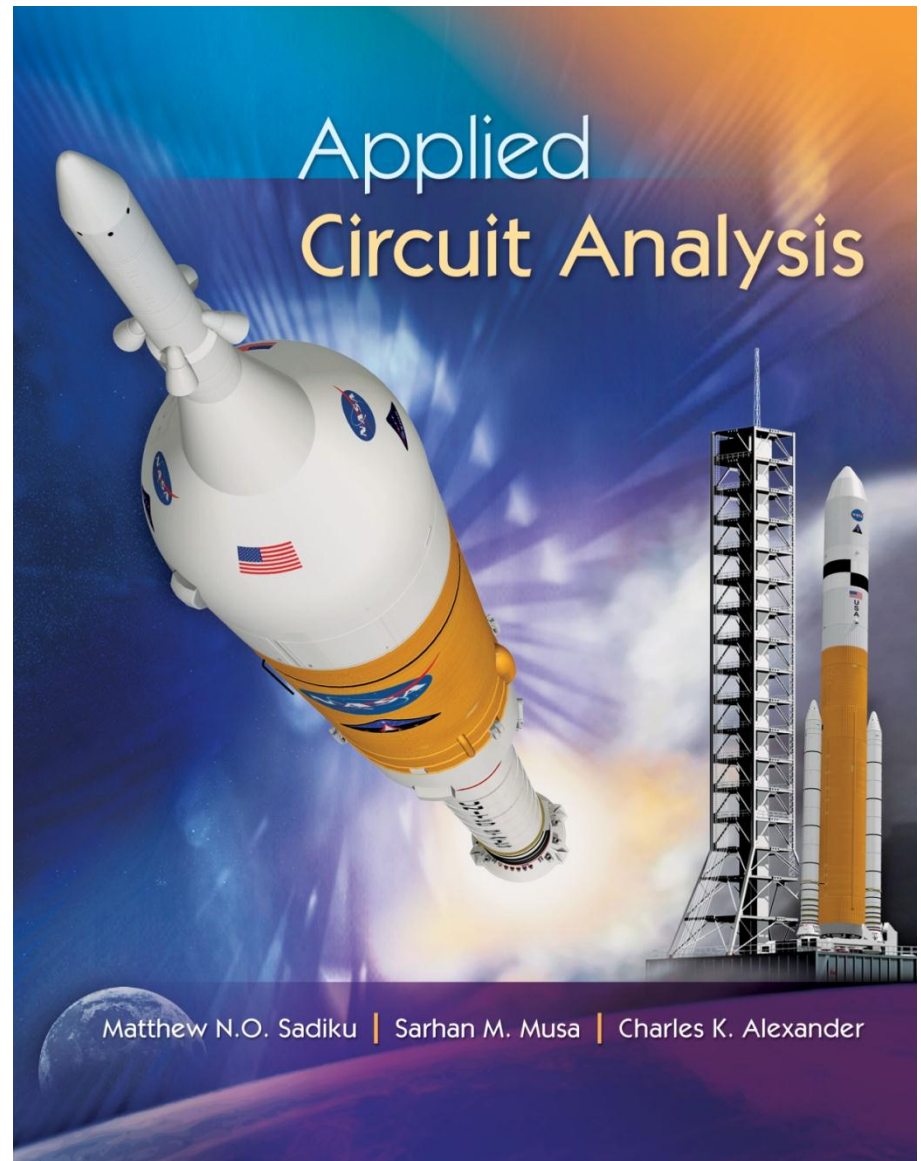


# Applied Circuit Analysis

## Chapter 10

### Inductance



Matthew N.O. Sadiku | Sarhan M. Musa | Charles K. Alexander

# Overview

- **This chapter will cover the inductor**
- **Like the capacitor, inductors do not dissipate energy**
- **The difference being that capacitors store their energy in electric fields and inductors use magnetic fields.**

# Electromagnetic Induction


- When a magnetic flux passes through a coil or conductor, an **electromotive force (emf)** is generated.
- This is known as **electromagnetic induction**.
- The emf produces a voltage at the terminals of the conductor.
- This is known as **Faraday's law**.

# Induction

- This can be expressed mathematically as:

$$v = N \frac{d\phi}{dt} = N \times \text{Rate of change in flux}$$

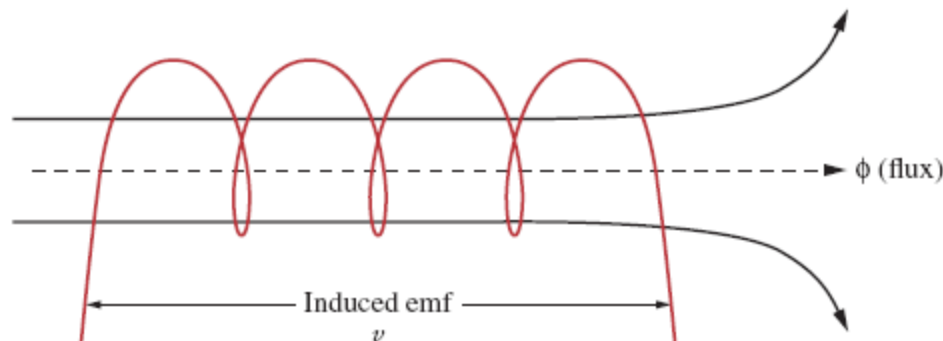- Where  $v$  is the induced voltage and  $N$  is the number of turns in the coil.



# Lenz's Law

- The polarity of the induced emf and the direction of the current flow can be determined by applying **Lenz's law:**
- The induced current always develops a flux that opposes the change producing the current.
- The combination of Faraday's law and Lenz's law allows us to calculate induced voltage and polarity.


# Inductors

- An **inductor** is a passive element that stores energy in its magnetic field
- They have applications in power supplies, transformers, radios, TVs, radars, and electric motors.
- Any conductor has inductance, but the effect is typically enhanced by coiling the wire up.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

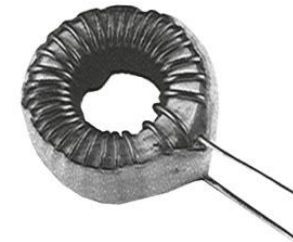

(b)



(c)

Courtesy of Tech America

# Inductors II

- If a current is passed through an inductor, the voltage across it is directly proportional to the time rate of change in current

$$v = L \frac{di}{dt}$$


- Where,  $L$ , is the unit of inductance, measured in Henries, H.
- One Henry is 1 volt-second per ampere.
- The voltage developed tends to oppose a changing flow of current.

# Inductors III

- Calculating the inductance depends on the geometry:
- For example, for a solenoid the inductance is:

$$L = \frac{N^2 \mu A}{l}$$

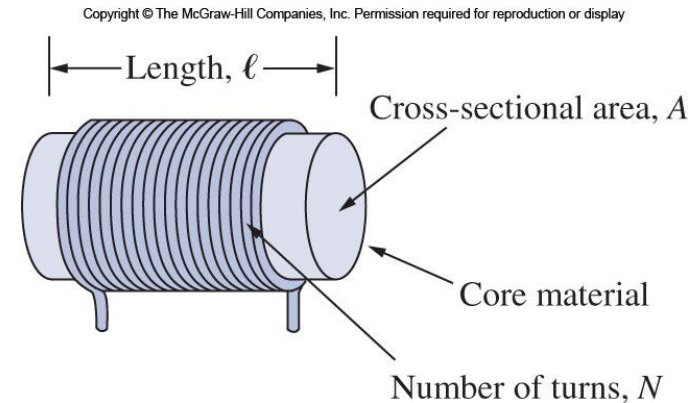- Where  $N$  is the number of turns of the wire around the core of cross sectional area  $A$  and length  $l$ .





# Permeability

- The material used for the core has a magnetic property called the permeability,  $\mu$ .
- **Permeability** is the ability of a material to support a magnetic flux.
- **Free space has a fixed permeability,  $\mu_0$**
- Other materials are compared to this by the **relative permeability  $\mu_r$**

# Permeability II

- The permeability of a material is the product of  $\mu_0$  and  $\mu_r$ .
- Here are the relative permeability of some common materials:

Relative permeability of some common materials\*.

Material	Relative permeability ( $\mu_r$ )
Air	1
Cobalt	250
Nickel	600
Soft iron	5,000
Silicon-iron	7,000
Nonmagnetic metals	1


\*The values given are typical; they vary from one published source to another owing to different varieties of most materials.

# Increasing Inductance

- There are a few ways to increase inductance:
  - Increase the number of turns
  - Increase the cross sectional area
  - Decrease the coil length
  - Change the core material
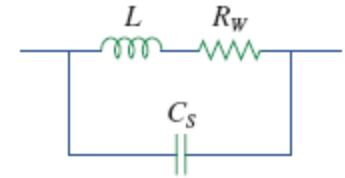
# Realistic Inductor

- Inductors in the real world have non-ideal behavior.
- Most significantly, being made of wire, they do not have zero resistance.
- What may be surprising is that they also have some capacitance due to the turns being insulated but adjacent to each other.



# Energy Storage

- The energy stored in an inductor's magnetic field is the average value of the current

$$W = v \times 0.5 I_m \times t$$

- The power delivered to the inductor is:

$$p = vi = \left( L \frac{di}{dt} \right) i$$

- The energy stored is:

$$w = \frac{1}{2} L I_m^2$$

# Properties of Inductors

- **If the current through an inductor is constant, the voltage across it is zero**
- **Thus an inductor acts like a short for DC**
- **The current through an inductor cannot change instantaneously**
- **If this did happen, the voltage across the inductor would be infinity!**
- **This is an important consideration if an inductor is to be turned off abruptly; it will produce a high voltage**

# Properties of Inductors II

- Like the ideal capacitor, the ideal inductor does not dissipate energy stored in it.
- Energy stored will be returned to the circuit later
- In reality, inductors do have internal resistance due to the wiring used to make them.
- A real inductor thus has a winding resistance in series with it.
- There is also a small winding capacitance due to the closeness of the windings
- These two characteristics are typically small, though at high frequencies, the capacitance may matter.

# Types of Inductors


- Inductors can range in value from  $\mu\text{H}$  to tens of Henries.
- The low values are used in communications systems, while the large values are used in power systems
- They may be fixed or variable
- The circuit symbol for fixed and variable inductors is shown here:





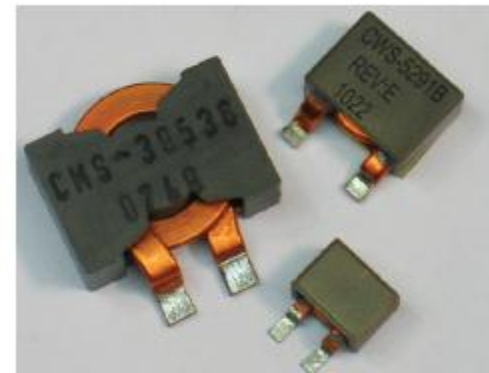
# Types of Inductors II

- Inductors are also referred to as chokes sometimes.
- They can be linear or toroidal, where the core is circular.


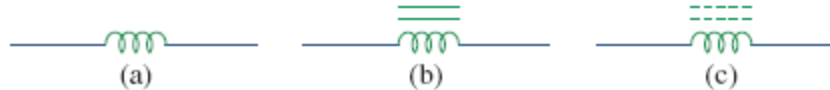
# Cores

- There are three common types of cores used in inductors: air (a), iron (b), and ferrite (c)





- The type of core used is determined by the application.
- Iron core inductors have large values associated with power applications.
- Air and ferrite cores are often used at high frequency.

# Series Inductors

- We now need to extend the series parallel combinations to inductors
- First, let's consider a series combination of inductors
- Applying KVL to the loop:

$$v = v_1 + v_2 + v_3 + \cdots + v_N$$

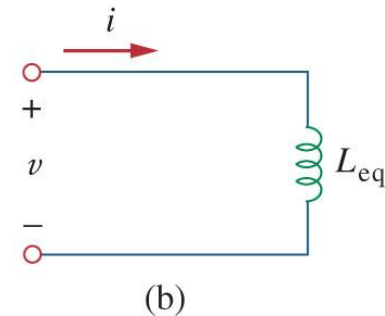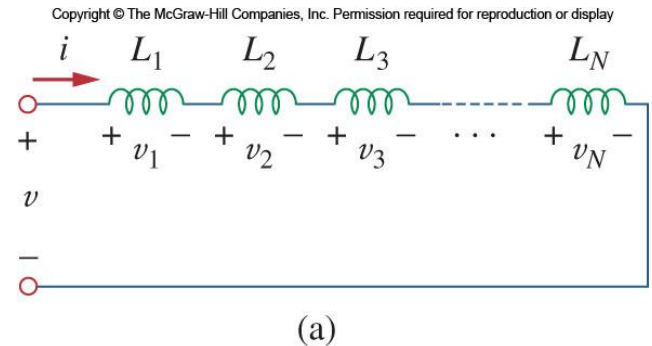

# Series Inductors II

- **Factoring in the voltage current relationship**

$$v_k = L_k \frac{di}{dt}$$

- **We get**

$$L_{eq} = L_1 + L_2 + L_3 + \cdots + L_N$$

- **Here we can see that the inductors have the same behavior as resistors.**
- **Therefore the equivalent inductance is the sum of the individual inductors.**


# Parallel Inductors

- Now consider a parallel combination of inductors:
- Using the same approach we did for resistors, the equivalent inductance will be:

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_N}$$

- For two inductors:


$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

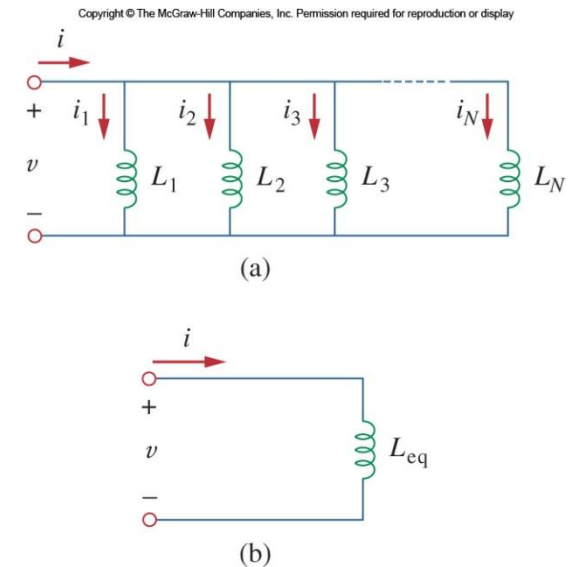

# Transient RL Circuits

- A RL circuit only contains resistors and inductors.
- Let us consider the circuit shown here:
- At  $t=0$  we will assume the inductor has an initial current.
- Applying KVL:

$$v_L + v_R = 0$$

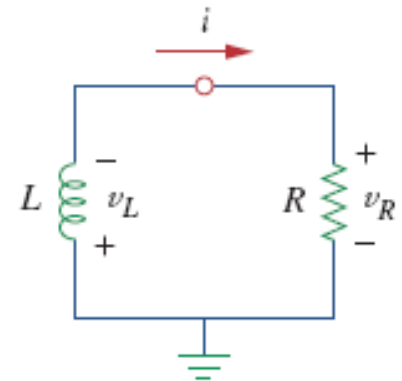

# Transient RL Circuits II

- Applying differential calculus shows that:

$$i(t) = I_0 e^{-Rt/L}$$


- The natural response of the RL circuit is an exponential decay.
- Much like the capacitor, there is a time constant:

$$\tau = \frac{L}{R}$$

# Transient RL Circuits III

- The time constant again has units of seconds.
- Knowing the current, we can say the voltage across the resistor is:

$$v_R(t) = I_0 R e^{-t/\tau}$$

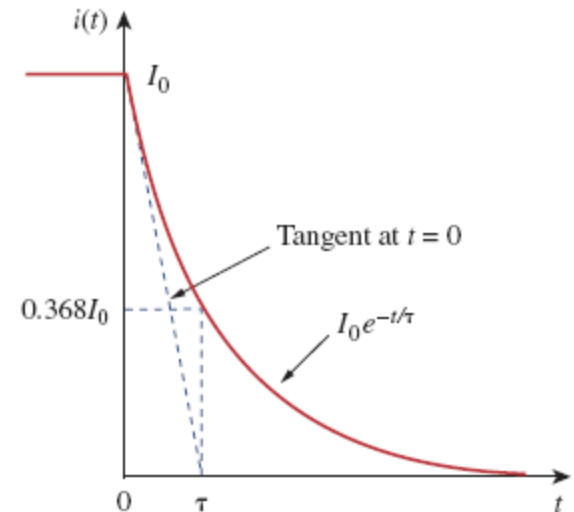



# Applications


- Due to their bulky size, inductors are less frequently used as compared to capacitors, however they have some applications where they are best suited.
- They can be used to create a large amount of current or voltage for a short period of time.
- Their resistance to sudden changes in current can be used for spark suppression.
- Along with capacitors, they can be used for frequency discrimination.

# Relays

- **Many applications of inductors are exploiting the magnetic field generated and the inductance is a side effect of using a coil of wires to create the field.**
- **A relay is a good example of this:**
- **A coil of wire is used to make an electromagnet.**
- **When energized the magnet moves a contact within a switch.**
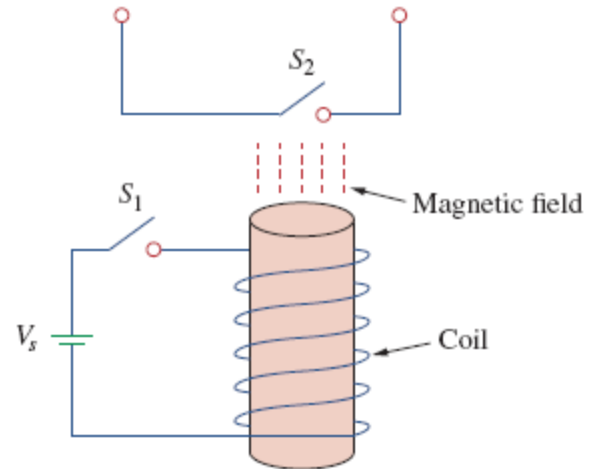
# Relays II

- Thus a relay is capable of opening or closing an isolated switch by way of current passing through the coil.
- This can enable a host of applications



# Relays III

- **The fact that the magnet has an inductance affects the behavior of the relay:**
- **The inductor's resistance to the introduction of current means that there will be a delay from when the current is applied to the time the contact moves.**

$$t_d = \tau \ln \frac{i(0) - i(\infty)}{i(t_d) - i(\infty)}$$

# Caution about Relays

- **Another side effect of using a relay is the inductance will generate a high voltage when the input current is turned on or off.**
- **This can damage some transistors or chips that are connected to the same circuit.**